



আন্তর্জাতিক ইসলামী বিশ্ববিদ্যালয় চট্টগ্রাম  
الجامعة الإسلامية العالمية شيتاغونغ  
International Islamic University Chittagong

**Department of Electrical and Electronic Engineering**

**Project Submission**

**Name of Project: Simple Audio Amplifier Using Single Transistor**

**Course Code : EEE-2302**

**Course Title : Electronics-I**

**Submitted by:**

**Name : 1. Shaila Akther Jesi (ET-241439)**  
**2. Nusrat Zubaira Kamal (ET-241440)**  
**3. Puja Dewanjee (ET-241442)**


**Submitted to:**

**Jubaida Nahar Tuli**  
**Assistant Lecturer EEE, IIUC**

**Date of submission: 21-02-2025**

## Project Name: LDR Darkness Sensor

### Circuit Diagram:

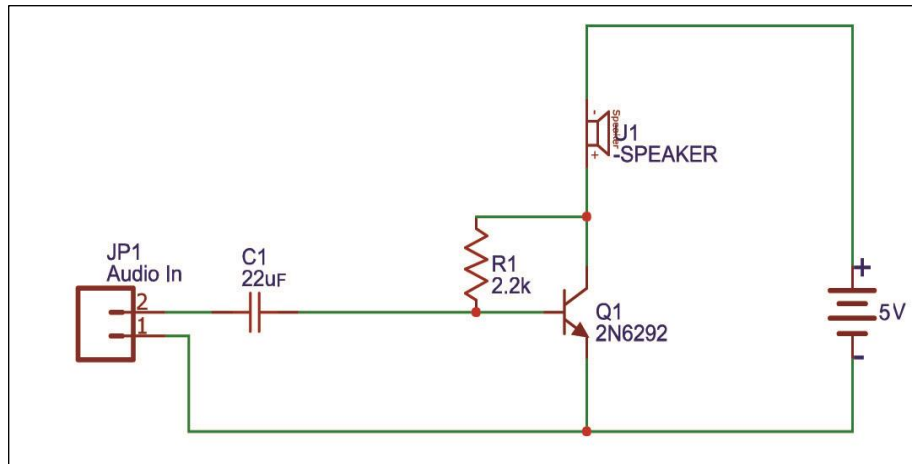

### Working Principal:

First place transistor on breadboard. Insert resistor at pin 1 and 2 of transistor. Insert positive terminal of capacitor at pin1 of transistor. Insert one wire of 3.5 mm jack at negative terminal of capacitor. Insert remain wire of 3.5 mm jack at pin3. Insert one wire of speaker at pin2. Connect remain wire of speaker to +5v supply. Connect ground of power supply to pin3. Plug the 3.5 mm jack to any audio playing device and enjoy the sound.

### **Equipment:**

1. 2N6292- Transistor
2. 2.2k- Resistor
3. 22uF- Capacitor
4. 3.5mm Jack
5. Speaker
6. Breadboard

### **Equipment Cost:**

| Equipment's Name   | Equipment Cost |
|--------------------|----------------|
| 2N6292- Transistor | 5 TK           |
| 2.2k- Resistor     | 2 TK           |
| 22uF- Capacitor    | 30 TK          |
| 3.5mm Jack         | 93 TK          |
| Speaker            | 40 TK          |
| Breadboard         | 155 TK         |
| <b>Total Cost</b>  | <b>325 TK</b>  |